

2013

CAPP

Paper- 1

Full Marks: 50

Time: 3 hours

Answer any five questions whereas Group-A will be compulsory

The figures in the right hand margin indicate marks

Candidates are required to give their answer in
their own words as far as practicable

GROUP-A

1. Choose the correct answers from the following:

1 x 10 =10

- i. A positive binary no. is represented by:
 - a. 0-sign bit
 - b. 1-sign bit
 - c. 2-sign bit
 - d. None of these
- ii. The sum of 11010 + 01111 equals:
 - a. 101001
 - b. 101010
 - c. 110101
 - d. 101000
- iii. An inverter performs an operation known as
 - a. Complementation
 - b. Assertion
 - c. Inversion
 - d. Both (a) and (c)
- iv. Which one of the following is not valid rule for Boolean algebra?
 - a. $A + 1 = 1$
 - b. $A = A'$
 - c. $A.A = A$
 - d. $A.1 = A$
- v. According to associative law of multiplication:
 - a. $B = B.B$
 - b. $A(BC) = (AB)C$
 - c. $A(A+1) = A$
 - d. $A+AB = A$

- vi. A 3-variable K-map has:
 - a. **Eight cells**
 - b. Three cells
 - c. Sixteen cell
 - d. Four cells
- vii. The device used to convert a binary no. to a 7-segment display format is:
 - a. Multiplexer
 - b. Encoder
 - c. **Decoder**
 - d. Register
- viii. The input to a full-adder are $A=1, B=1, C_{in}=0$. The output are:
 - a. $\Sigma=1, C_{out}=1$
 - b. $\Sigma=1, C_{out}=0$
 - c. **$\Sigma=0, C_{out}=1$**
 - d. $\Sigma=0, C_{out}=0$
- ix. A flip flop is in toggle condition the:
 - a. $J=1, K=0$
 - b. **$J=1, K=1$**
 - c. $J=0, K=0$
 - d. $J=0, K=1$
- x. Asynchronous counter is known as:
 - a. **Ripple counter**
 - b. Multiple clock counter
 - c. Decade counter
 - d. Modulus

GROUP-B


Answer any four of the following:

2. (a) Find the 10's complement of 54. 2
 (b) Convert the following: 4
 - I. $(110101)_2 = (?)_{10}$
 - II. $(16.125)_{10} = (?)_2$
 - III. $(6A5C)_{16} = (?)_2$
 - IV. $(1204)_8 = (?)_{10}$
- (c) What do you mean by logic gates? Describe their basic types. 4
3. (a) Define the three basic law of Boolean algebra. 3
 (b) Show that 2

$$(A+B)(A+C)=A+BC$$
- (c) What is the difference between minterm and maxterm? 5
4. (a) Simplify the 5

$$AB+A.(B+C)+B.(B+C)$$
- (b) Show the K-map 5
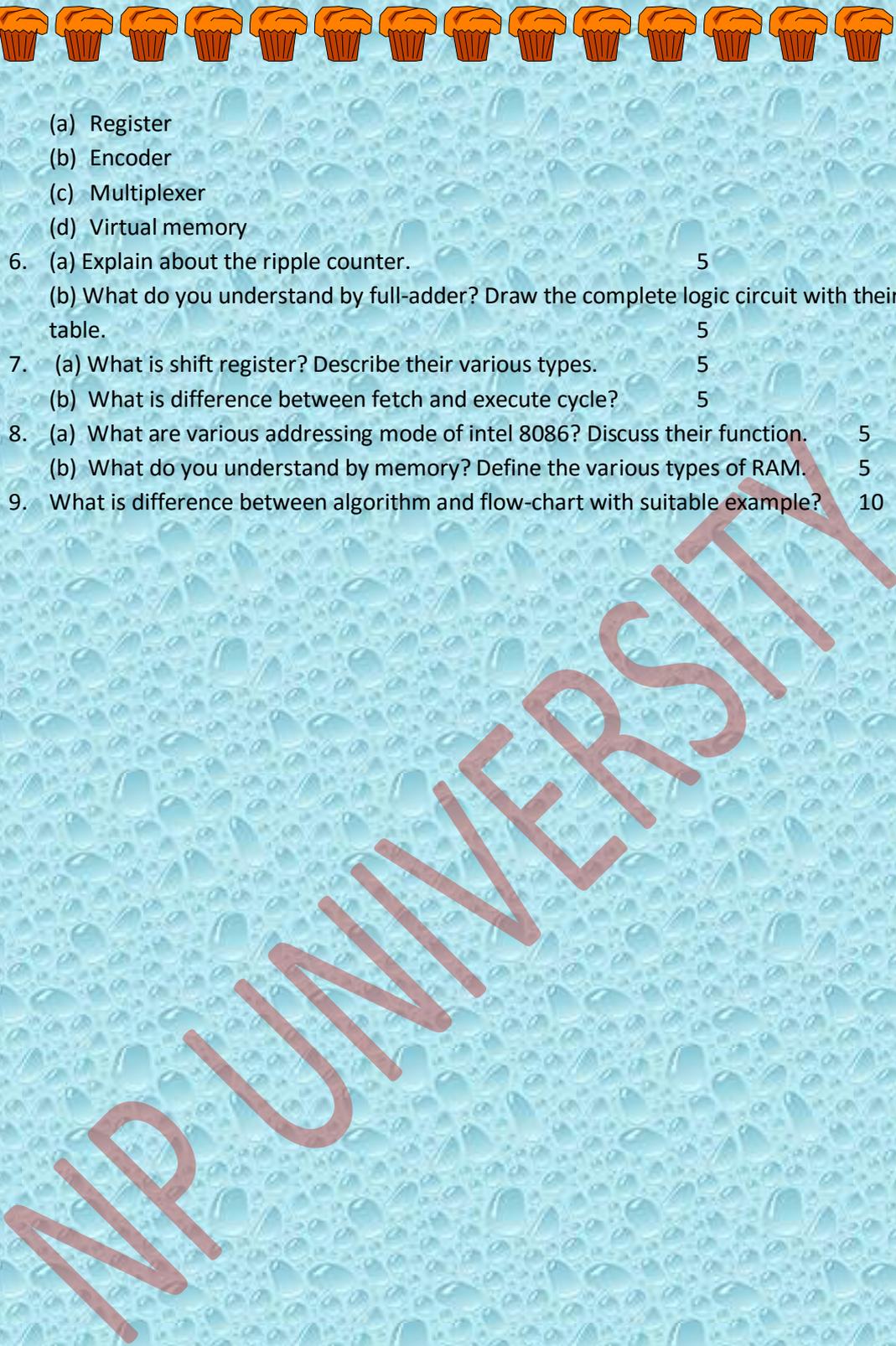
$$F(ABCD)=\Sigma(0,1,2,3,5,7,8,10,14)$$
5. Write short notes of any two: 2 X 5=10



- (a) Register
 - (b) Encoder
 - (c) Multiplexer
 - (d) Virtual memory
6. (a) Explain about the ripple counter. 5
(b) What do you understand by full-adder? Draw the complete logic circuit with their truth table. 5
7. (a) What is shift register? Describe their various types. 5
(b) What is difference between fetch and execute cycle? 5
8. (a) What are various addressing mode of intel 8086? Discuss their function. 5
(b) What do you understand by memory? Define the various types of RAM. 5
9. What is difference between algorithm and flow-chart with suitable example? 10

